

## Lab 3

**Môn:** Hệ thống số (TN)

**Lớp:** L01

**Nhóm:** 7

**GVHD:** Kiều Đỗ Nguyên Bình

<b>Thành viên:</b> Lê Đức Huy	1810166
Nguyễn Gia Huy	1810173
Huỳnh Thiên Trình	1810615
Lê Bá Thông	1810555
Lê Duy Bình	51204735

### 1 Introduction

#### 1.1 Aims

- Implement half adder, full adder circuit.
- Practice with different adder circuits.

#### 1.2 Requirements

- Understand how to implement an adder circuit.
- Have ability to combine the small circuits to implement the bigger ones.

#### 1.3 Procedure

- Verify the gates.
- Make the connections as per the circuit diagram.
- Switch on  $V_{cc}$  and apply various combinations of input according to the truth table.
- Note down the output readings for half/full adder and half/full subtractor sum/difference and the carry/borrow bit for different combinations of inputs.

#### 1.4 Report Requirements

Your report of each exercise should include:

- Answer and explain all questions (If required).
- The circuit and truth table of each exercise.
- Two or Three photos of the circuit **on KIT**.

## 2 Contents

### 2.1 Half/Full Adder

#### 2.1.1 Using X-OR and Basic Gates

##### Half Adder

 


Figure 1: Half Adder circuit with X-OR and Basic Gates.

##### Full Adder

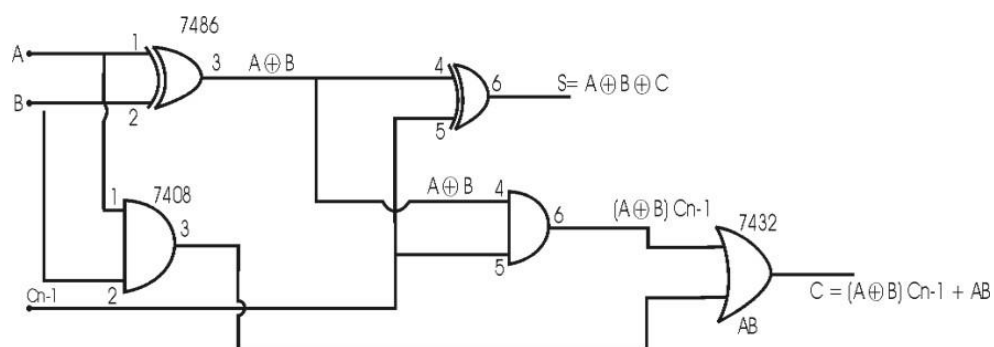


Figure 2: Full Adder circuit with X-OR and Basic Gates.

#### 2.1.2 Using only NAND gates

##### Half Adder

 


Figure 3: Half Adder circuit with only NAND gates.

## Full Adder

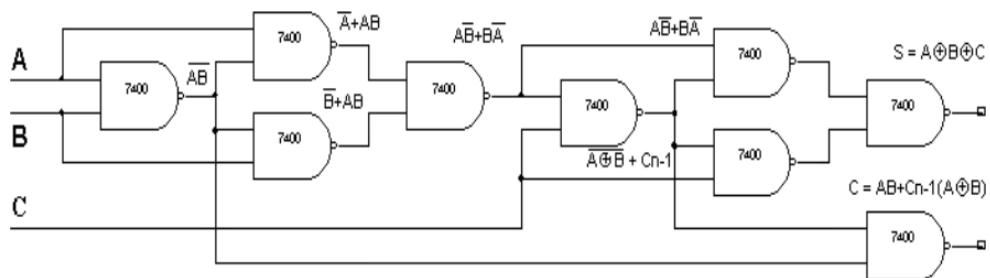


Figure 4: Full Adder circuit with only NAND gates.

## 2.2 Half/Full Subtractor

### 2.2.1 Using X-OR and Basic Gates

#### Half Subtractor

 


Figure 5: Half Subtractor circuit with X-OR and Basic Gates.

#### Full Subtractor

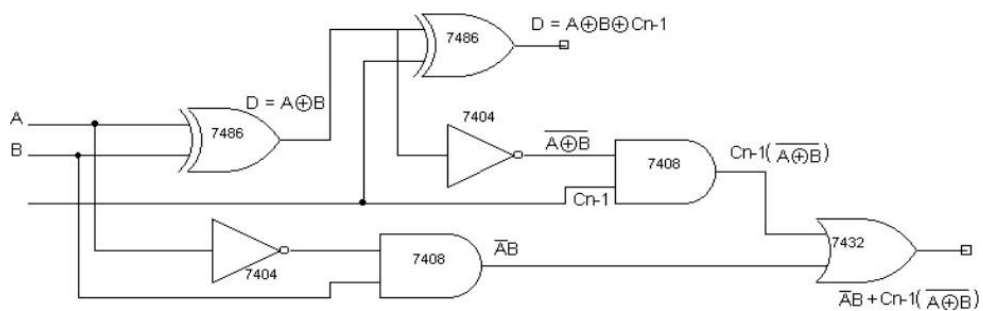


Figure 6: Full Subtractor circuit with X-OR and Basic Gates.

### 2.2.2 Using only NAND gates

#### Half Subtractor

 


Figure 7: Half Subtractor circuit with only NAND gates.

#### Full Subtractor

 


Figure 8: Full Subtractor circuit with only NAND gates.

Fill in these tables:

Half Adder					
A	B	S	C	S(V)	C(V)
0	0	0	0	0	0
0	1	1	0	1	0
1	0	1	0	1	0
1	1	0	1	0	1


Half Subtractor					
A	B	D	B	D(V)	B(V)
0	0	0	0	0	0
0	1	1	1	1	1
1	0	1	0	1	0
1	1	0	0	0	0

Full Adder						
A	B	Cn-1	S	C	S(V)	C(V)
0	0	0	0	0	0	0
0	0	1	1	0	1	0
0	1	0	1	0	1	0
0	1	1	0	1	0	1
1	0	0	1	0	1	0
1	0	1	0	1	0	1
1	1	0	0	1	0	1
1	1	1	1	1	1	1


Full Subtractor						
A	B	Cn-1	D	B	D(V)	B(V)
0	0	0	0	0	0	0
0	0	1	1	1	1	1
0	1	0	1	1	1	1
0	1	1	0	1	0	1
1	0	0	1	0	1	0
1	0	1	0	0	0	0
1	1	0	0	0	0	0
1	1	1	1	1	1	1



### 3 Exercises

 **Exercise 1:** Implement a half subtractor circuit use **only** NAND gate. Show results on LED diode.



Half Subtractor					
A	B	D	B	D(V)	B(V)
0	0	0	0	0	0
0	1	1	1	1	1
1	0	1	0	1	0
1	1	0	0	0	0

 


  




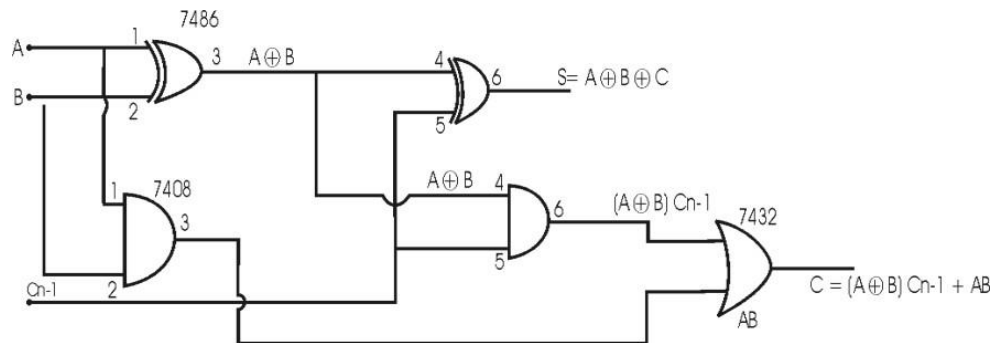**Exercise 2: Implement full adder circuit from the half adder**



The full adder circuit must have 3 inputs: bit A, bit B and carry bit. Show results on LED diode.




Full Adder						
A	B	$C_{n-1}$	S	C	S(V)	C(V)
0	0	0	0	0	0	0
0	0	1	1	0	1	0
0	1	0	1	0	1	0
0	1	1	0	1	0	1
1	0	0	1	0	1	0
1	0	1	0	1	0	1
1	1	0	0	1	0	1
1	1	1	1	1	1	1

 



  

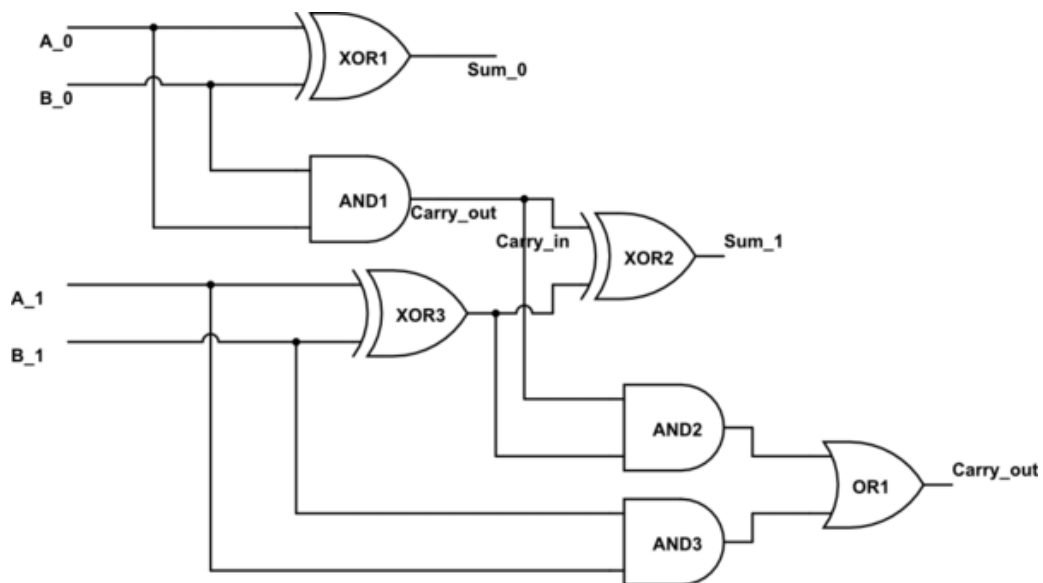**Exercise 3:** Implement an adder that can work out the sum of two 2-bits numbers by using full adder circuit. Show results on both LED diot and 7-seg LED.



Inputs				Outputs		
a <sub>1</sub>	a <sub>0</sub>	b <sub>1</sub>	b <sub>0</sub>	c <sub>1</sub>	s <sub>1</sub>	s <sub>0</sub>
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	0	0	1	0
0	0	1	1	0	1	1
0	1	0	0	0	0	1
0	1	0	1	0	1	0
0	1	1	0	0	1	1
0	1	1	1	1	0	0
1	0	0	0	0	1	0
1	0	0	1	0	1	1
1	0	1	0	1	0	0
1	0	1	1	1	0	1
1	1	0	0	0	1	1
1	1	0	1	1	0	0
1	1	1	0	1	0	1
1	1	1	1	1	1	0



