


dce 2018



Digital Systems

Arithmetic

BK TP.HCM

dce 2018

Introduction

- Digital circuits are frequently used for arithmetic operations
- Fundamental arithmetic operations on binary numbers and digital circuits which perform arithmetic operations will be examined.

BK TP.HCM

2

dce 2018

Binary Addition

- Binary numbers are added like decimal numbers.
- In decimal, when numbers sum more than 9 a carry results.
- In binary when numbers sum more than 1 a carry takes place.
- Addition is the basic arithmetic operation used by digital devices to perform subtraction, multiplication, and division.

BK TP.HCM

3

dce 2018

Binary Addition

- $0 + 0 = 0$
- $1 + 0 = 1$
- $1 + 1 = 0 + \text{carry } 1$
- $1 + 1 + 1 = 1 + \text{carry } 1$
- E.g.:

1010	(10)	001	(1)
+1100	(12)	+101	(5)
10110	(22)	+111	(7)
		1101	(13)

BK TP.HCM

4

dce
2018

Representing Signed Numbers

- Since it is only possible to show magnitude with a binary number, the sign (+ or -) is shown by adding an extra “sign” bit.
- A sign bit of 0 indicates a positive number.
- A sign bit of 1 indicates a negative number.
- The 2’s complement system is the most commonly used way to represent signed numbers.

5

dce
2018

Representing Signed Numbers

- So far, numbers are assumed to be unsigned (i.e. positive)
- How to represent signed numbers?
- Solution 1: Sign-magnitude - Use one bit to represent the sign, the remain bits to represent magnitude

7

6

0

0 = +ve

1 = -ve

s

magnitude

+27 = 0001 1011 b

-27 = 1001 1011 b

 - Problem: need to handle sign and magnitude separately.
- Solution 2: One’s complement - If the number is negative, invert each bits in the magnitude

+27 = 0001 1011 b

-27 = 1110 0100 b

 - Not convenient for arithmetic - add 27 to -27 results in 1111 1111_b
 - Two zero values

6

dce
2018

Representing Signed Numbers

- Solution 3: Two’s complement - represent negative numbers by taking its magnitude, invert all bits and add one:

Positive number

+27 = 0001 1011b

Invert all bits

1110 0100b

Add 1

-27 = 1110 0101b

2⁷

2⁶

2⁰
- Unsigned number

2⁷

2⁶

2⁰
- Signed 2’s complement

s

$$x = -b_{N-1}2^{N-1} + b_{N-2}2^{N-2} + \dots + b_12^1 + b_02^0$$

7

dce
2018

Examples of 2’s Complement

- A common method to represent -ve numbers:
 - use half the possibilities for positive numbers and half for negative numbers
 - to achieve this, let the MSB have a negative weighting
- Construction of 2’s Complement Numbers
 - 4-bit example


Decimal	2’s Complement (Signed Binary)			
	-8	+4	+2	+1
5	0	1	0	1
-5	1	0	1	1
7	0	1	1	1
-3	1	1	0	1

8

Why 2's complement representation?

- If we represent signed numbers in 2's complement form, subtraction is the same as addition to negative (2's complemented) number.
 
$$\begin{array}{r}
 27 \text{ } 0001 \text{ } 1011 \text{ b} \\
 - 17 \text{ } 0001 \text{ } 0001 \text{ b} \\
 \hline
 + 10 \text{ } 0000 \text{ } 1010 \text{ b} \\
 \\
 + 27 \text{ } 0001 \text{ } 1011 \text{ b} \\
 + - 17 \text{ } 1110 \text{ } 1111 \text{ b} \\
 \hline
 + 10 \text{ } 0000 \text{ } 1010 \text{ b}
 \end{array}$$



- Note that the range for 8-bit unsigned and signed numbers are different.
- 8-bit unsigned: **0 +255**
- 8-bit 2's complement signed number: **-128 +127**



9

Comparison Table

- Note the **"wrap-around"** effect of the binary representation
 - i.e. The top of the table wraps around to the bottom of the table


Unsigned	Binary	2' comp
7	0111	7
6	0110	6
5	0101	5
4	0100	4
3	0011	3
2	0010	2
1	0001	1
0	0000	0
15	1111	-1
14	1110	-2
13	1101	-3
12	1100	-4
11	1011	-5
10	1010	-6
9	1001	-7
8	1000	-8



10

Sign Extension

 - How to translate an 8-bit 2's complement number to a 16-bit 2's complement number?



- This operation is known as **sign extension**.



11

Sign Extension

- Sometimes we need to extend a number into more bits
- Decimal
 - converting 12 into a 4 digit number gives 0012
 - we add 0's to the left-hand side
- Unsigned binary
 - converting 0011 into an 8 bit number gives 00000011
 - we add 0's to the left-hand side
- For signed numbers we duplicate the sign bit (MSB)
- Signed binary
 - converting 0011 into 8 bits gives 00000011 (duplicate the 0 MSB)
 - converting 1011 into 8 bits gives 11111011 (duplicate the 1 MSB)
 - Called **"Sign Extension"**



12

Representing Signed Numbers

- In order to change a binary number to 2's complement it must first be changed to 1's complement.
 - To convert to 1's complement, simply change each bit to its complement (opposite).
 - To convert 1's complement to 2's complement add 1 to the 1's complement.
- A positive number is true binary with 0 in the sign bit.
- A negative number is in 2's complement form with 1 in the sign bit.
- A number is negated when converted to the opposite sign.
- A binary number can be negated by taking the 2's complement of it.



13

Signed Addition

- The same hardware can be used for 2's complement signed numbers as for unsigned numbers
 - this is the main advantage of 2's complement form
- Consider 4 bit numbers:
 - the Adder circuitry will "think" the negative numbers are 16 greater than they are in fact
 - but if we take only the 4 LSBs of the result (i.e. ignore the carry out of the MSB) then the answer will be correct providing it is with the range: -8 to +7.
- To add 2 n-bit signed numbers without possibility of overflow we need to:
 - sign extend to n+1 bits
 - use an n+1 bit adder



14

Addition in the 2's Complement System


- Perform normal binary addition of magnitudes.
- The sign bits are added with the magnitude bits.
- If addition results in a carry of the sign bit, the carry bit is ignored.
- If the result is positive it is in pure binary form.
- If the result is negative it is in 2's complement form.



15

Addition in the 2's Complement System

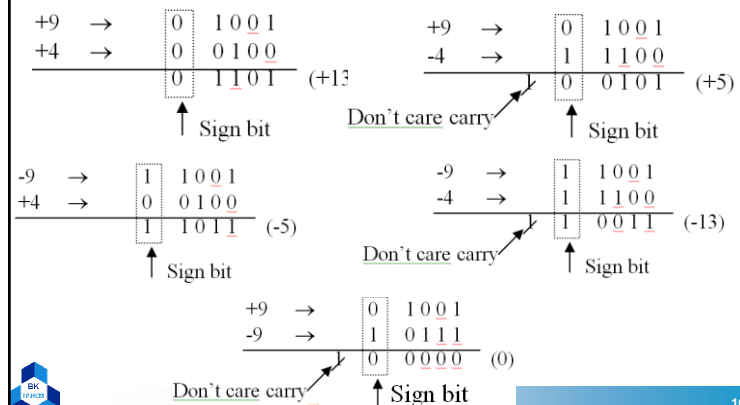- Perform normal binary addition of magnitudes.



16

Subtraction in the 2's Complement System

- The number subtracted (subtrahend) is negated.
- The result is added to the minuend.
- The answer represents the difference.
- If the answer exceeds the number of magnitude bits an overflow results.

$$\begin{array}{r}
 +9 \rightarrow \begin{array}{|c|} \hline 0 \\ \hline \end{array} 1001 \\
 +8 \rightarrow \begin{array}{|c|} \hline 0 \\ \hline \end{array} 1000 \\
 \hline
 \begin{array}{|c|} \hline 1 \\ \hline \end{array} 0001 \\
 \uparrow \text{Sign bit}
 \end{array}$$



17

Multiplication and Division by 2^N

- In decimal, multiplying by 10 can be achieved by
 - shifting the number left by one digit adding a zero at the LS digit
- In binary, this operation multiplies by 2
- In general, left shifting by N bits multiplies by 2^N
 - zeros are always brought in from the right-hand end
 - E.g.

Binary	Decimal
1101	13
11010	26
110100	52



18

Multiplication of Binary Numbers

- This is similar to multiplication of decimal numbers.
- Each bit in the multiplier is multiplied by the multiplicand.
- The results are shifted as we move from LSB to MSB in the multiplier.
- All of the results are added to obtain the final product.

$$\begin{array}{r}
 1001 \quad (9) \\
 \times 1011 \quad (11) \\
 \hline
 1001 \\
 0000 \\
 1001 \\
 \hline
 1100011 \quad (99)
 \end{array}$$



19

Binary Division

- This is similar to decimal long division.
- It is simpler because only 1 or 0 are possible.
- The subtraction part of the operation is done using 2's complement subtraction.
- If the signs of the dividend and divisor are the same the answer will be positive.
- If the signs of the dividend and divisor are different the answer will be negative.



20

Summary of Signed and Unsigned Numbers

Unsigned	Signed
MSB has a positive value (e.g. +8 for a 4-bit system)	MSB has a negative value (e.g. -8 for a 4-bit system)
The carry-out from the MSB of an adder can be used as an extra bit of the answer to avoid overflow	To avoid overflow in an adder, need to sign extend and use an adder with one more bit than the numbers to be added
To increase the number of bits, add zeros to the left-hand side	To increase the number of bits, sign extend by duplicating the MSB
Complementing and adding 1 converts X to (2N - X)	Complementing and adding 1 converts X to -X

21

BCD Addition

- When the sum of each decimal digit is less than 9, the operation is the same as normal binary addition.
- When the sum of each decimal digit is greater than 9, a binary 6 is added. This will always cause a carry.

47	0100	0111	→	47 BCD
+35	+ 0011	0101	→	35 BCD
82	0111	1100	→	invalid
	+ 1	0110	→	+ 6
	1000	0010	→	valid

22

Hexadecimal Arithmetic


- Hex addition:
 - Add the hex digits in decimal.
 - If the sum is 15 or less express it directly in hex digits.
 - If the sum is greater than 15, subtract 16 and carry 1 to the next position.
- Hex subtraction – use the same method as for binary numbers.
- When the MSD in a hex number is 8 or greater, the number is negative. When the MSD is 7 or less, the number is positive.

3AF	592 ₍₁₆₎ - 3A5 ₍₁₆₎ FFF - 3A5 = C5A
+23C	C5A + 1 = C5B is 2's complement of 3A5
5EB	
	592
	+ C5B
	1ED

23

Arithmetic Circuits

 - An arithmetic/logic unit (ALU) accepts data stored in memory and executes arithmetic and logic operations as instructed by the control unit.



24

Arithmetic Circuits

- Typical sequence of operations:
 - Control unit is instructed to add a specific number from a memory location to a number stored in the accumulator register.
 - The number is transferred from memory to the B register.
 - Number in B register and accumulator register are added in the logic circuit, with sum sent to accumulator for storage.
 - The new number remains in the accumulator for further operations or can be transferred to memory for storage.



Binary Addition


- Recall the binary addition process

$$\begin{array}{r} A \ 1 \ 0 \ 0 \ 1 \\ + \ B \ 0 \ 0 \ 1 \ 1 \\ \hline S \ 1 \ 1 \ 0 \ 0 \end{array}$$
- LS Column has 2 inputs 2 outputs
 - Inputs: A₀ B₀
 - Outputs: S₀ C₁
- Other Columns have 3 inputs, 2 outputs
 - Inputs: A_n B_n C_n
 - Outputs: S_n C_{n+1}
 - We use a "half adder" to implement the LS column
 - We use a "full adder" to implement the other columns
 - Each column feeds the next-most-significant column.



Parallel Binary Adder

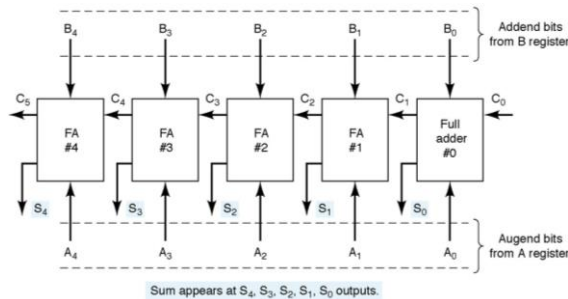- The A and B variables represent 2 binary numbers to be added. The C variables are the carries. The S variables are the sum bits.




Half Adder

- Truth Table

A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

- Boolean Equations $S = \bar{A}B + A\bar{B} = A \oplus B$
- $C = AB$


- Implementation

 

Full Adder

• Truth Table

Augend bit input	Addend bit input	Carry bit input	Sum bit output	Carry bit output
A	B	C _{IN}	S	C _{OUT}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 

• Boolean Equations

$$S = \bar{A}\bar{B}C_i + \bar{A}B\bar{C}_i + A\bar{B}\bar{C}_i + AB C_i$$

$$= A \oplus B \oplus C_i$$

$$C_o = \bar{A}BC_i + A\bar{B}C_i + ABC_i + AB\bar{C}_i$$

$$= AB + AC_i + BC_i$$

$$= AB + C_i(A + B)$$

K maps for the full-adder outputs.

	\bar{C}_{IN}	C_{IN}
$\bar{A}\bar{B}$	0	1
$\bar{A}B$	1	0
AB	0	1
$A\bar{B}$	1	0

K map for S

$$S = \bar{A}\bar{B}C_{IN} + \bar{A}B\bar{C}_{IN} + AB C_{IN} + A\bar{B}\bar{C}_{IN}$$

(a)


	\bar{C}_{IN}	C_{IN}
$\bar{A}\bar{B}$	0	0
$\bar{A}B$	0	1
AB	1	1
$A\bar{B}$	0	1

K map for C_{OUT}

$$C_{OUT} = BC_{IN} + AC_{IN} + AB$$

(b)

Circuitry for a full adder

 


Full Adder from Half Adders


• Truth Table

A	B	HA _s	HA _c	C _i	S	C _o
0	0	0	0	0	0	0
0	0	0	0	1	1	0
0	1	1	0	0	1	0
0	1	1	0	1	0	1
1	0	1	0	0	1	0
1	0	1	0	1	0	1
1	1	0	1	0	0	1
1	1	0	1	1	1	1

• Boolean Equations

 

Adder Example

 


Hierarchy

- Any Verilog design you do will be a module
- This includes testbenches!
- Interface (“black box” representation)
 - Module name, ports
- Definition
 - Describe functionality of the block
 - Includes interface
- Instantiation
 - Use the module inside another module


Hierarchy

- Build up a module from smaller pieces
 - Primitives
 - Other modules (which may contain other modules)
- Design: typically top-down
- Verification: typically bottom-up

Full Adder Hierarchy

 


Add_half Module

 

```
module Add_half(c_out, sum, a, b);
  output sum, c_out;
  input a, b;

  xor sum_bit(sum, a, b);
  and carry_bit(c_out, a, b);
endmodule
```

Add_full Module

 

```

module Add_full(c_out, sum, a, b, c_in) ;
  output sum, c_out;
  input a, b, c_in;
  wire w1, w2, w3;

  Add_half AH1(.sum(w1), .c_out(w2), .a(a), .b(b));
  Add_half AH2(.sum(sum), .c_out(w3), .a(c_in), .b(w1));
  or carry_bit(c_out, w2, w3);
endmodule

```



37

Can Mix Styles In Hierarchy!

```

module Add_half_bhv(c_out, sum, a, b);
  output reg sum, c_out;
  input a, b;
  always @(a, b) begin
    sum = a ^ b;
    c_out = a & b;
  end
endmodule

module Add_full_mix(c_out, sum, a, b, c_in) ;
  output sum, c_out;
  input a, b, c_in;
  wire w1, w2, w3;
  Add_half_bhv AH1(.sum(w1), .c_out(w2), .a(a), .b(b));
  Add_half_bhv AH2(.sum(sum), .c_out(w3), .a(c_in), .b(w1));
  assign c_out = w2 | w3;
endmodule

```



38

Full Adder: RTL/Dataflow

```

module fa_rtl (A, B, CI, S, CO) ;

  input A, B, CI ;
  output S, CO ;

  // use continuous assignments
  assign S = A ^ B ^ CI;
  assign CO = (A & B) | (A & CI) | (B & CI);

endmodule

```



39

Full Adder: Behavioral

- Circuit “reacts” to given events (for simulation)
 - Actually list of signal changes that affect output

```

module fa_bhv (A, B, CI, S, CO) ;

  input A, B, CI;
  output S, CO;
  reg S, CO; // explained in later lecture – “holds” values

  // use procedural assignments
  always@(A or B or CI)
  begin
    S = A ^ B ^ CI;
    CO = (A & B) | (A & CI) | (B & CI);
  end
endmodule


```



40

Parallel Adder

 
- Uses 1 full adder per bit of the numbers
- The carry is propagated from one stage to the next most significant stage
 - takes some time to work because of the carry propagation delay which is n times the propagation delay of one stage.



Complete Parallel Adder With Registers

- Register notation – to indicate the contents of a register we use brackets:
 - [A]=1011 is the same as $A_3=1, A_2=0, A_1=1, A_0=1$
- A transfer of data to or from a register is indicated with an arrow
 - [B]→[A] means the contents of register B have been transferred to register A.
- Eg.: 1001 + 0101 using the parallel adder:
 - t1 : A CLR pulse is applied
 - t2 : 1001 from mem-→ B
 - t3 : 1001 + 0000 → A
 - t4 : 0101 from mem-→ B
 - t5 : The sum outputs → A
 - The sum of the two numbers is now present in the accumulator.

Complete Parallel Adder With Registers

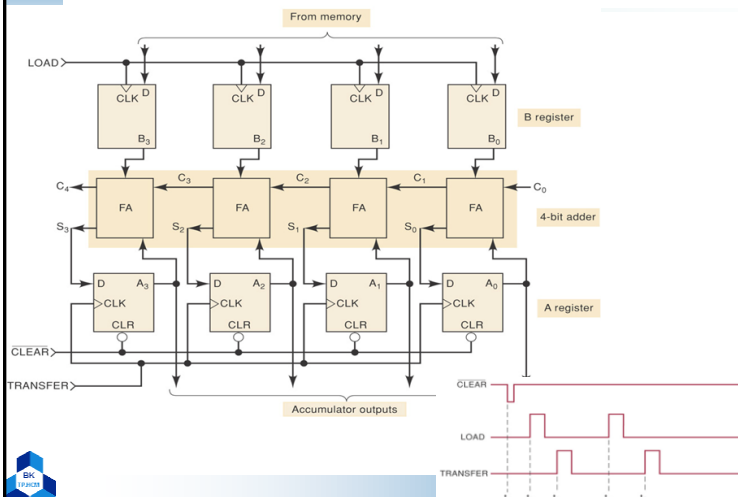

Carry Propagation

- Parallel adder speed is limited by carry propagation (also called **carry ripple**).
- Carry propagation results from having to wait for the carry bits to “ripple” through the device.
- Additional bits will introduce more delay.
- Various techniques have been developed to reduce the delay. The **look-ahead carry** scheme is commonly used in high speed devices.

dce 2018

Design a carry look-ahead adder

$$C1 = [A0 B0 + A0 C0 + B0 C0]$$

$$C2 = (A1 B1 + A1 C1 + B1 C1) = A1 B1 + (A1 + B1)[C1]$$

$$C3 = A2 B2 + A2 C2 + B2 C2$$

$$C3 = A2 B2 + (A2 + B2) \{A1 B1 + (A1 + B1) [A0 B0 + B0 C0 + A0 C0]\}$$

Final expression for C3 can be put into S-of-P form by multiplying all terms out. This results in a circuit with TWO levels of gating. The arrangement of Figure 6.9 requires that A0, B0, and C0 propagate through as many as 6 levels of gates before producing C3.

BK FRANKS

45

dce 2018

Integrated Circuit Parallel Adder

- The most common parallel adder is a 4 bit device with 4 interconnected FAs and look-ahead Carry circuits.
- Parallel adders may be cascaded together as shown to add larger numbers

BK FRANKS

46

dce 2018

Parallel adder used to add and subtract numbers in 2's-complement system.

BK FRANKS

47

dce 2018

2's Complement Addition using 1's Complement Operands

Parallel adder used to perform subtraction ($A - B$) using the 2's-complement system. The bits of the subtrahend (B) are inverted (1's complement), and $C_0 = 1$ to produce the 2's complement

BK FRANKS

48

dce 2018 Parallel adder/subtractor using the 2's-complement system

ADD = 1, SUB = 0:
B register passes to adder and Carry in = 0

ADD = 0, SUB = 1:
Complement of B register passes to adder and Carry in = 1

Transfer pulse

dce 2018 ALU Integrated Circuits

Function Table

S ₂	S ₁	S ₀	Operation	Comments
0	0	0	CLEAR	F ₃ F ₂ F ₁ F ₀ = 0000
0	0	1	B minus A	Needs C _N = 1
0	1	0	A minus B	Needs C _N = 0
0	1	1	A plus B	Needs C _N = 0
1	0	0	A ⊗ B	Exclusive-OR
1	0	1	A + B	OR
1	1	0	AB	AND
1	1	1	PRESET	F ₃ F ₂ F ₁ F ₀ = 1111

Notes: S inputs select operation.
OVR = 1 for signed-number overflow.

(b)

- ALUs can perform different arithmetic and logic functions as determined by a binary code on the function select inputs.

dce 2018 Two 74HC382 ALU chips connected as an eight-bit adder

Notes: Z1 adds lower-order bits.
Z2 adds higher-order bits.
Σ₇-Σ₀ = 8-bit sum.
OVR of Z2 is 8-bit overflow indicator.